

# Tutorial 6

## Problems of Combinational Logic

### **Exercise 1 Polling Report**

Four shop stewards ( $A$ ,  $B$ ,  $C$ ,  $D$ ) represent the following number of votes respectively: 100 votes, 150 votes, 250 votes and 175 votes. A proposal needs at least 50 % of the votes to be accepted. Write down the most simplified expression of a logic function ( $S$ ) that is 1 when a proposal is accepted and 0 when it is rejected. Draw the circuit diagram.

**Indication:** ' $A = 1$ ' means that the  $A$  shop steward accepts a proposal and ' $A = 0$ ' means that he or she rejects it. The same goes for the other shop stewards.

### **Exercise 2 Liquid Level**

Let us consider two tanks:  $R1$  and  $R2$ . The liquid level of each tank is checked by two sensors: a high-level sensor ( $A$  for  $R1$ ,  $B$  for  $R2$ ) and a low-level sensor ( $C$  for  $R1$ ,  $D$  for  $R2$ ). The values of  $A$ ,  $B$ ,  $C$ ,  $D$  are 1s when there is some liquid in front of the sensor; otherwise they are 0s. Three indicator lights ( $V1$ ,  $V2$ ,  $V3$ ) are set according to the following conditions:

- $V1 = 1$ , if  $R1$  and  $R2$  are full.
- $V2 = 1$ , if  $R1$  and  $R2$  are empty.
- $V3 = 1$ , in any other cases.

Write down the truth tables and the most simplified expressions of the outputs. Draw the circuit diagram.